

Part-17 - Problems & Solutions

②  $\frac{1}{2} + \frac{1}{2} + \frac{1}{2} + \frac{1}{2} = \frac{1}{G}$

⇒  $2 = \frac{1}{G}$

$G = \frac{1}{2} = 0.5$



⑥  $Q = 10 \text{ mC}$  ,  $C = 10 \mu\text{F}$  ,  $V = ?$

$V = \frac{Q}{C}$   $[\because Q = CV]$

$= \frac{10 \times 10^{-3}}{10 \times 10^{-6}}$

$V = 1 \text{ kV}$



⑦  $C = 10 \mu\text{F}$  ,  $V = 500 \text{ V}$  ,  $W = ?$

$W = \frac{1}{2} CV^2$  joules

$W = \frac{1}{2} \times 10 \times 10^{-6} \times 500 \times 500 = \underline{\underline{1.25 \text{ J}}}$



⑩  $C = 10 \text{ pF}$  ,  $V = 10 \text{ kV}$  ,  $Q = ?$

$Q = CV$

$= 10 \times 10^{-12} \times 10 \times 10^3$

$= 100 \times 10^{-9}$

$= \underline{\underline{0.1 \mu\text{C}}}$

$$(11) C_T = C_1 + C_2 + C_3 \dots = 2 + 2 + 2 + 2 = \underline{8 \mu F}$$

$$(12) V_L = 12V, V_R = 5V, V = ?$$

for pure RL circuit phasor diagram



$$V = \sqrt{V_R^2 + V_L^2}$$

$$= \sqrt{5^2 + 12^2} = \sqrt{169} = \underline{13 \text{ volts}}$$

\_\_\_\_\_ x \_\_\_\_\_

$$(14) \left[ \frac{10 \times 15}{10 + 15} \right] + 12 = R_{eq}$$

$$= \frac{150}{25} + 12 = \underline{18 \Omega}$$

\_\_\_\_\_ x \_\_\_\_\_

$$(15) R_{eq} = \frac{R_1 \cdot R_2}{R_1 + R_2} = \frac{\left(\frac{1}{3}\right) \left(\frac{1}{4}\right)}{\frac{1}{3} + \frac{1}{4}} = \frac{\frac{1}{12}}{\frac{7}{12}} = \underline{\underline{\frac{1}{7}}}$$

\_\_\_\_\_ x \_\_\_\_\_